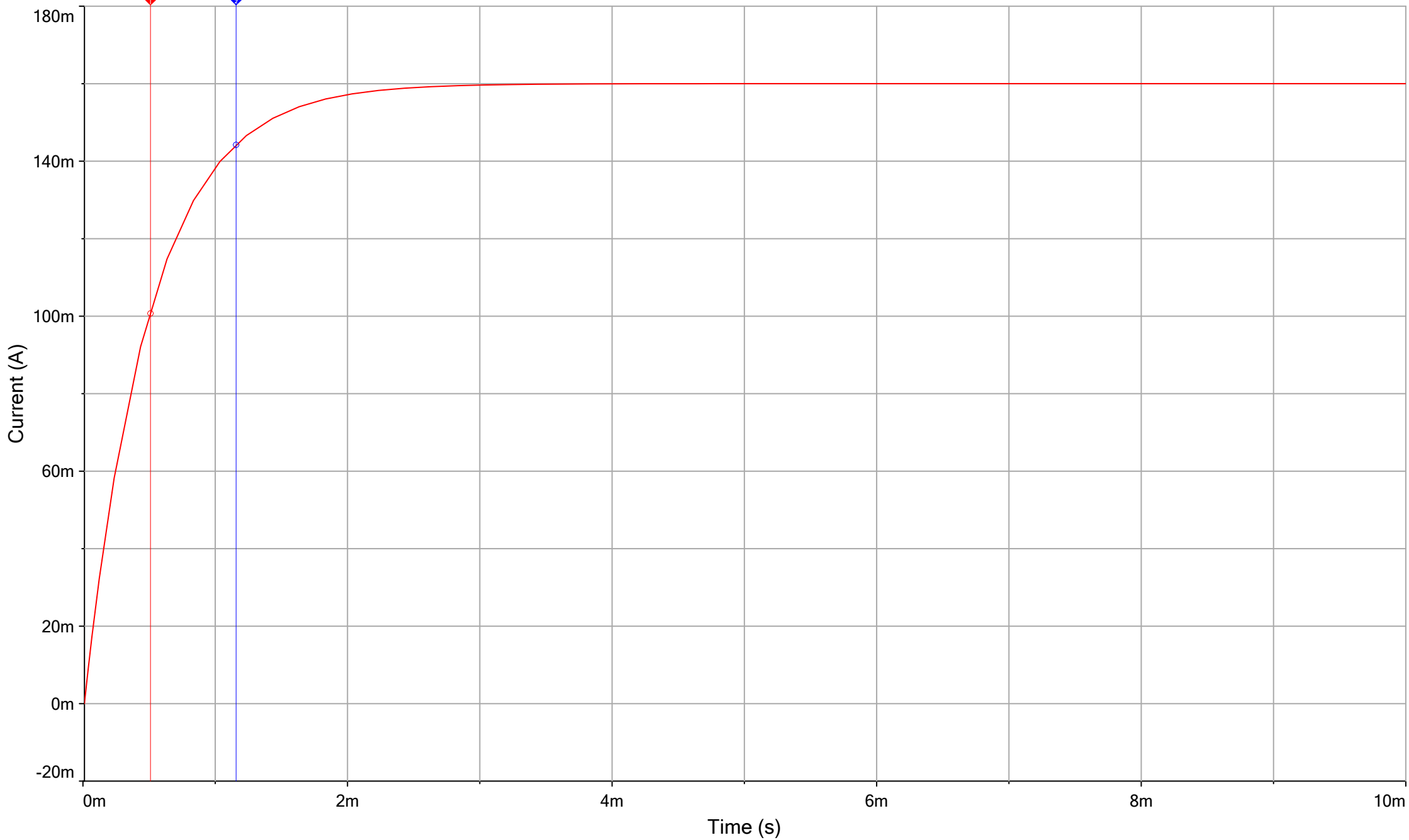


Circuito 1

Printing Time: martes, 14 de octubre de 2025, 10:35:21

Corriente



☒ $-I(L1:2)$
☐ $I(PR1)$

	x1	y1	x2	y2	dx	dy	dy/dx	1/dx
-I(L1:2) I(PR1):	500.0000μ	100.5557m	1.1481m	144.0000m	648.1285μ	43.4443m	67.0304	1.5429k